

Design of the Driving System of the Engine of Electrical Vehicle

Presented By

Md. Ohiduzzaman Sajol (2003043)
Amit Kumar Das (2003056)
Md. Washim Molla (2003058)
S.M. Fahim Shahriar (2003059)
Md. Mustafijur Rahman (2003057)
Sadman Shamyó (2003060)

Presented To

Dr. Md. Habibullah
Professor, Dept. of EEE, KUET
Md. Sajjad Hossain
Lecturer, Dept. of EEE, KUET

Presented On

November 10, 2025



Outline

- **Abstract**
- **Introduction**
- **Methodology**
- **List of Apparatus**
- **Model Description**
- **Results**
- **Conclusion**

Abstract

- **PECs replace engine parts, driving the green energy shift.**
- **EVs use DC-AC inverters and DC-DC converters for power control.**
- **An H-bridge converter model controls motor speed and torque.**
- **Novel diode placement ensures current continuity and energy recovery.**
- **MATLAB® GUI enables remote monitoring and control.**

Introduction: H-Bridge

- Figure 1 shows the **MOSFET-based H-bridge** motor drive.
- Four switches (Q1–Q4) **control motor direction and speed**.
- Flyback diodes (D1–D4) **protect against voltage spikes**.
- Diodes provide a **path for current** when switches are **off**.
- Stored energy can **feed back to supply** or **dissipate through a resistor**.

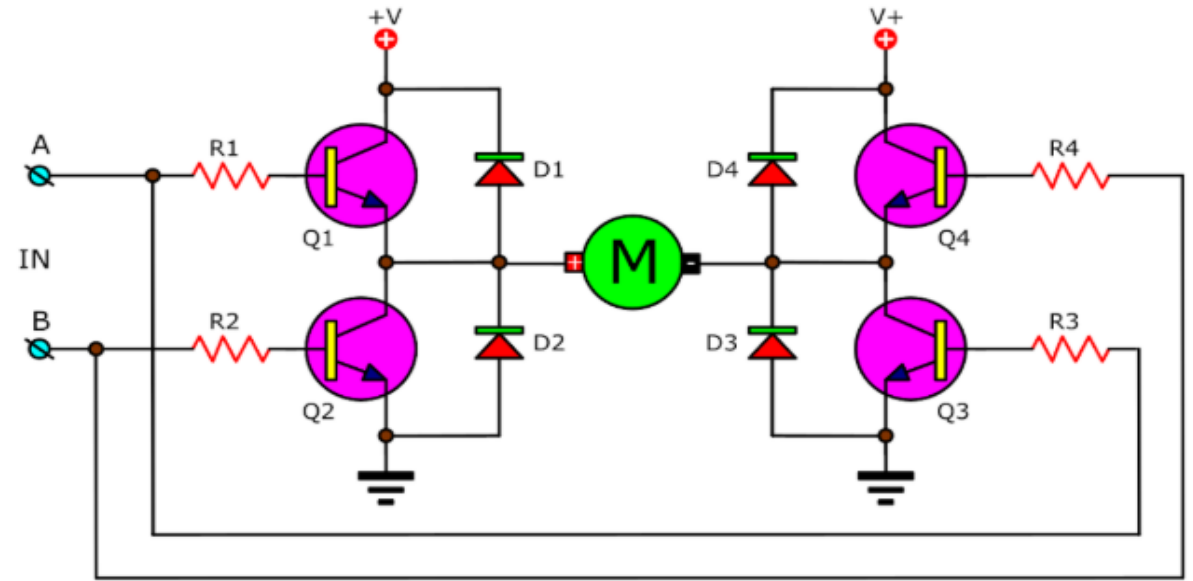


Figure 1: H-bridge DC motor drive [3]

Introduction: Motor Speed & Torque Control

- $Speed = K_s \times \frac{V - I_a R_a}{\phi}$ (in rpm)
- $Torque = \frac{60 \times E_b I_a}{2\pi \times speed}$ (in Nm)
- **Figure 2** compares speed control by armature resistance vs. DC-DC converter.
- Resistance control **wastes energy**; H-bridge PWM control is **efficient**.
- Speed and torque are regulated by adjusting **supply voltage and back emf (E_b)**.

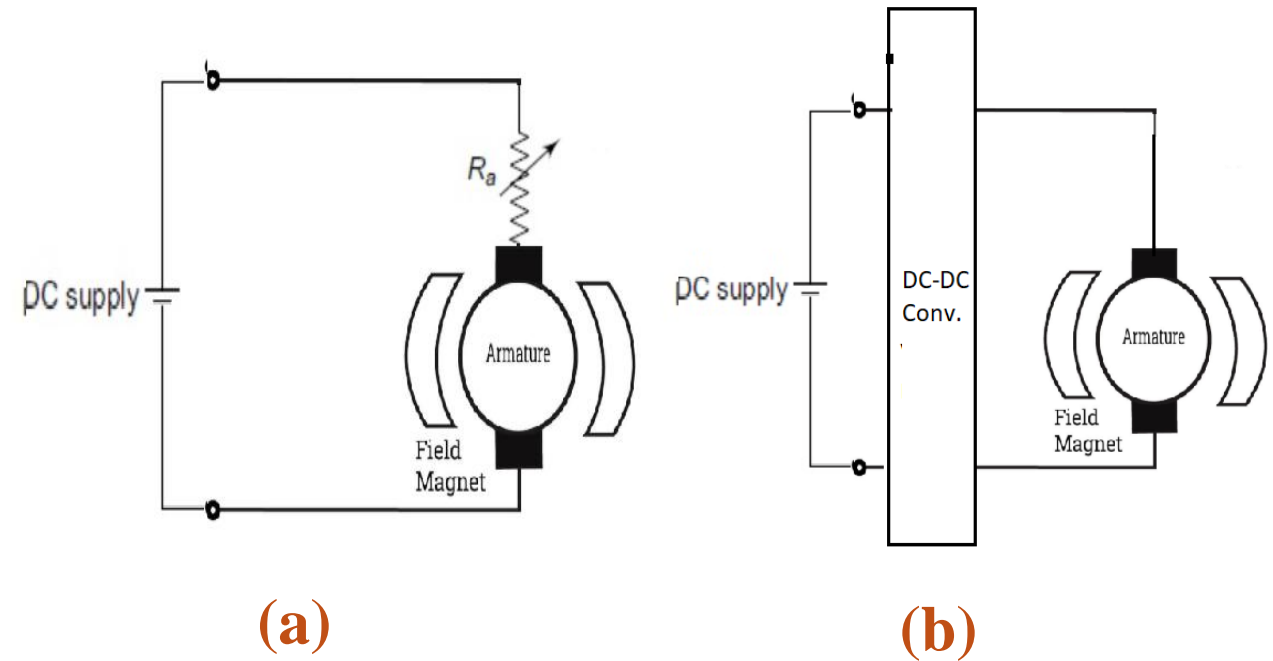


Figure 2: (a) DC motor speed control by varying armature resistance and (b) by using a DC-DC converter

Introduction: PID Controller in Closed Loop Operation

- **Figure 3** illustrates the motor speed control using a **PID feedback loop**.
- The PID controller compares **actual speed** with the **set point**.
- It adjusts the motor input to **minimize speed error** and maintain stability.


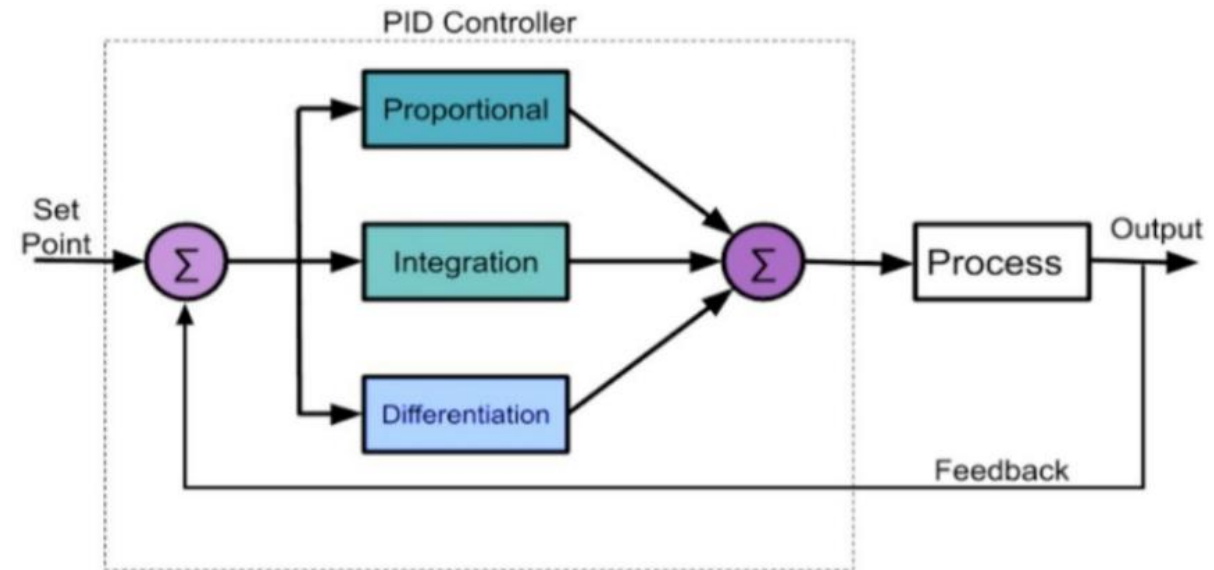


Figure 3: Block diagram of PID controller [5]

Methodology: Project Flow Chart

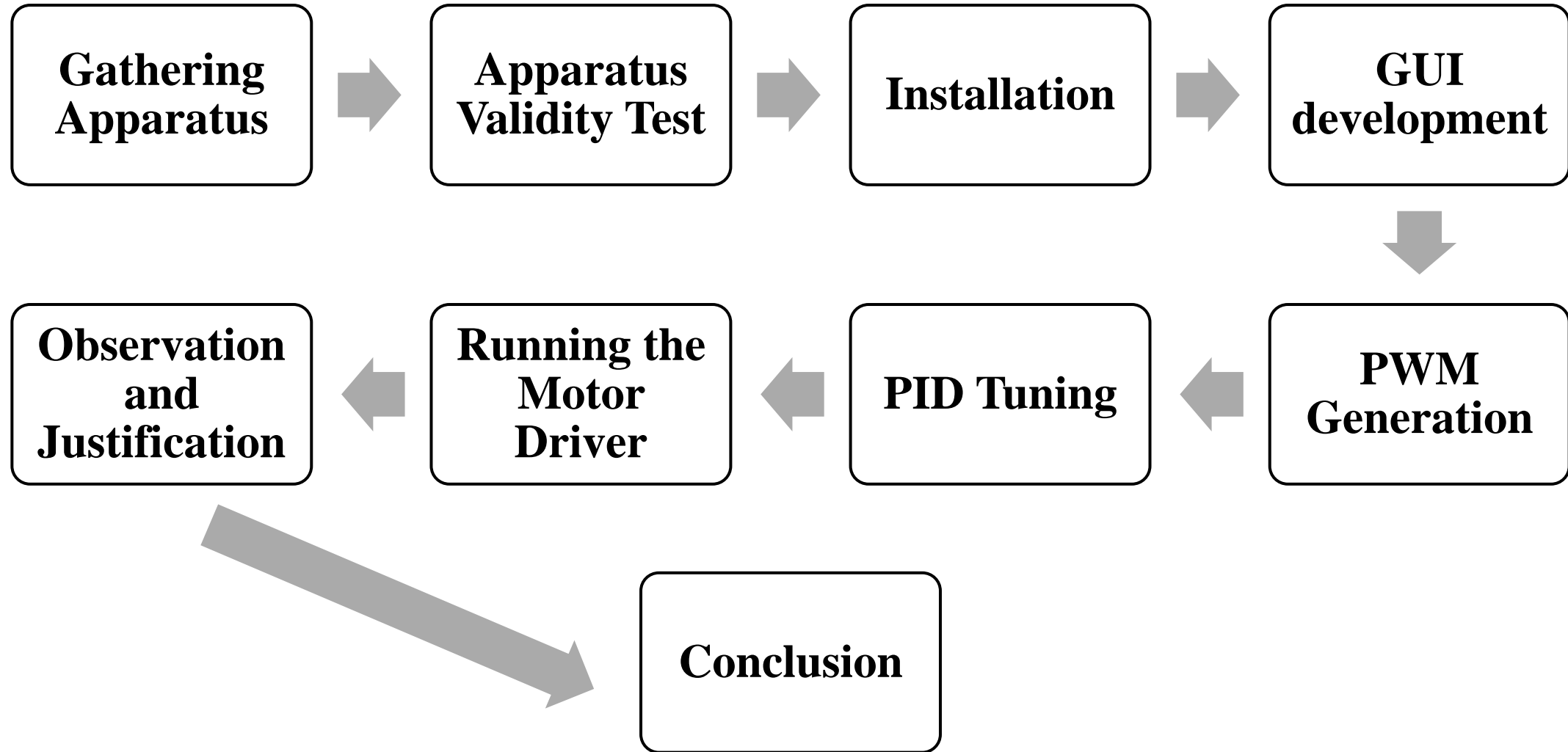

Methodology: Execution Steps

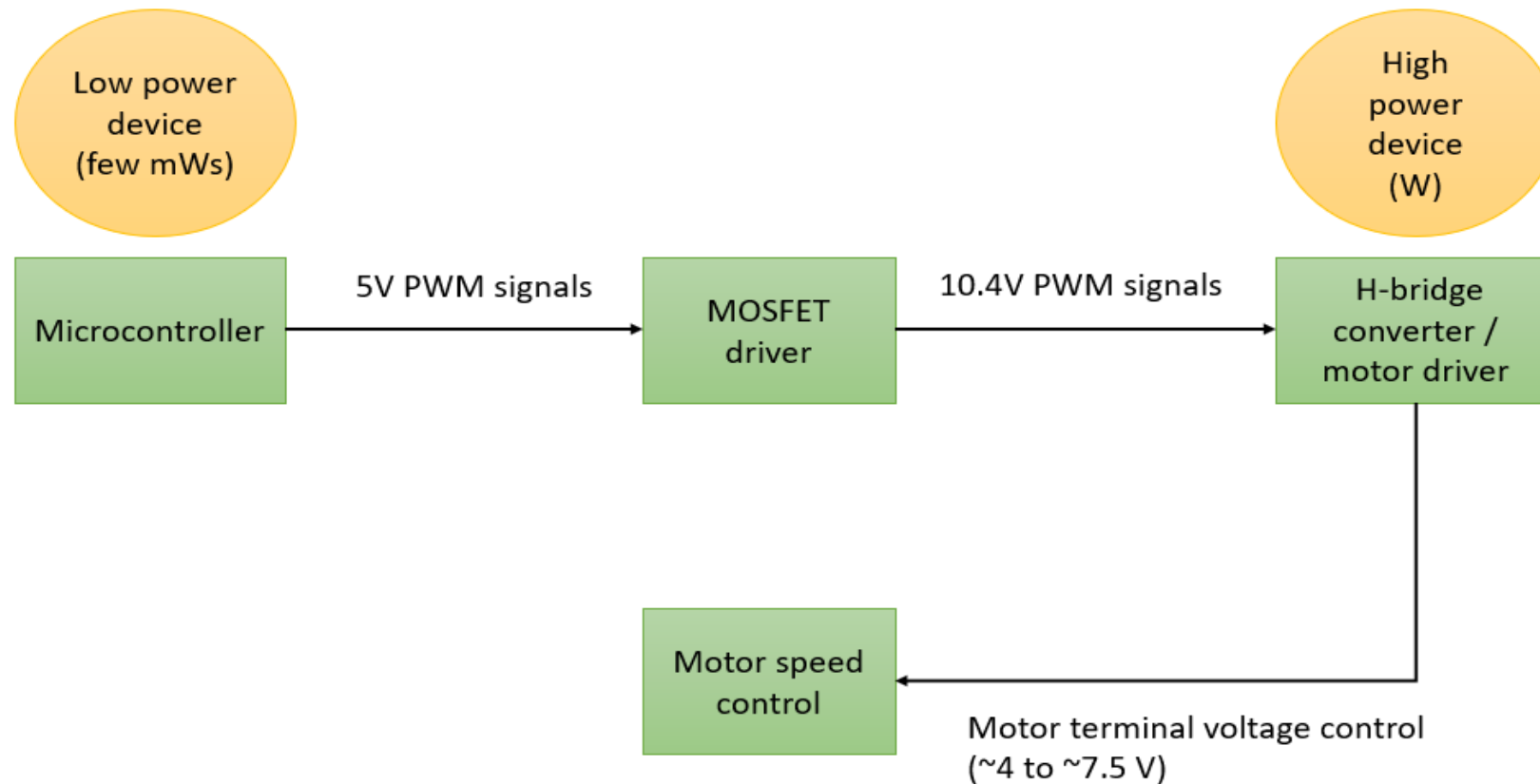


Figure 4: Execution steps to motor drive modelled for EV

Methodology: Pretesting Apparatus

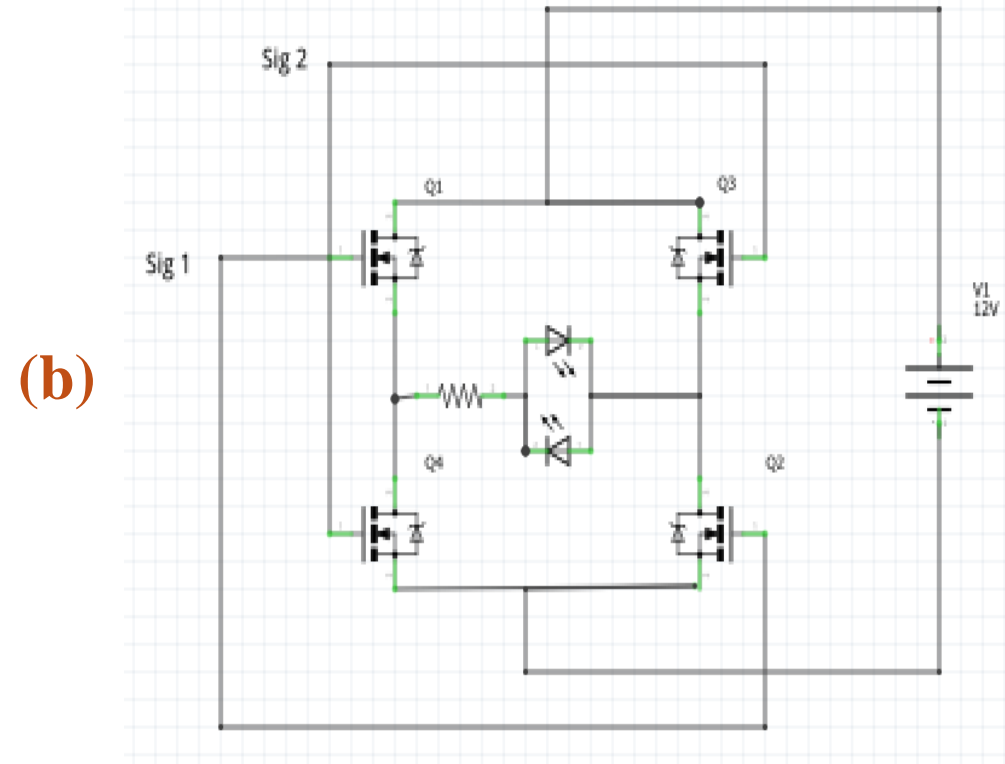
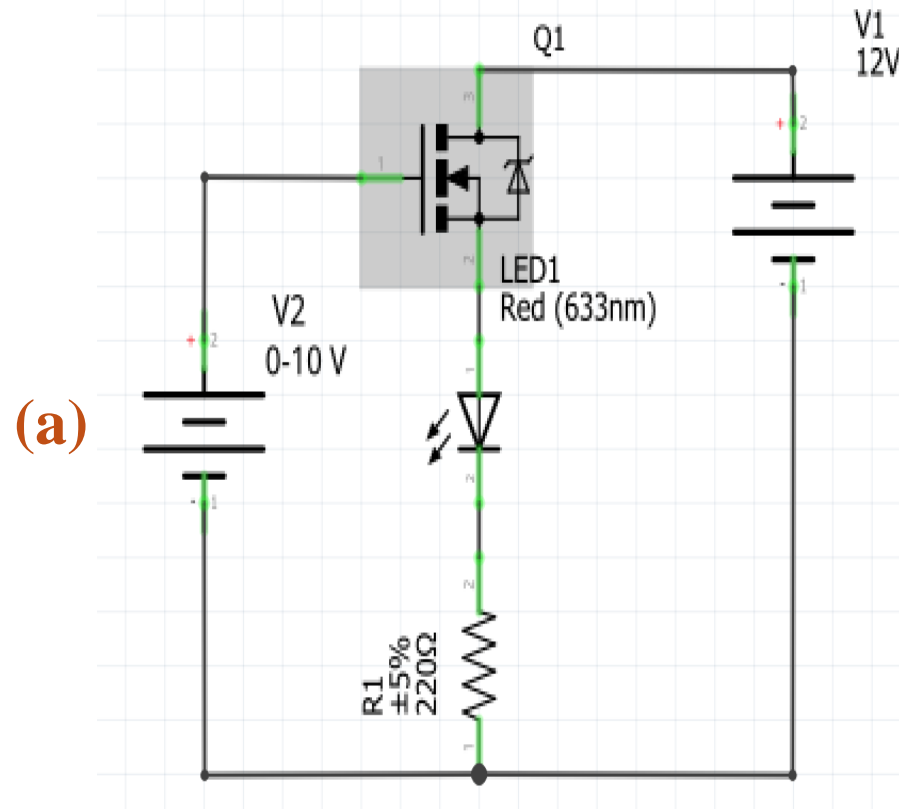


Figure 5: (a) MOSFET operability test — LED turns on at $V_{GS}=10$ V; off at lower V_{GS} . (b) Driver and H-bridge validity test — LEDs indicate correct operation based on Sig 1 and Sig 2 logic states.

Methodology: GUI Development

```
Command Window

Starting Application
Sent to Arduino: POWER_ON
Arduino replied: 0,0,0,0.68,1.846

Arduino replied: 0,0,0,0.60,2.301

Connected and live updating started.
Sent to Arduino: FORWARD
Sent to Arduino: POWER_ON
Connected and live updating started.
Sent to Arduino: REVERSE
Sent to Arduino: OPEN_LOOP
Arduino replied: 1,1,1,0.60,1.540

Arduino replied: 1,1,0,0.60,2.065

Sent to Arduino: POWER_ON
Connected and live updating started.
Sent to Arduino: SHUTDOWN
fx >>
```

Figure 6: Acknowledgement from Arduino

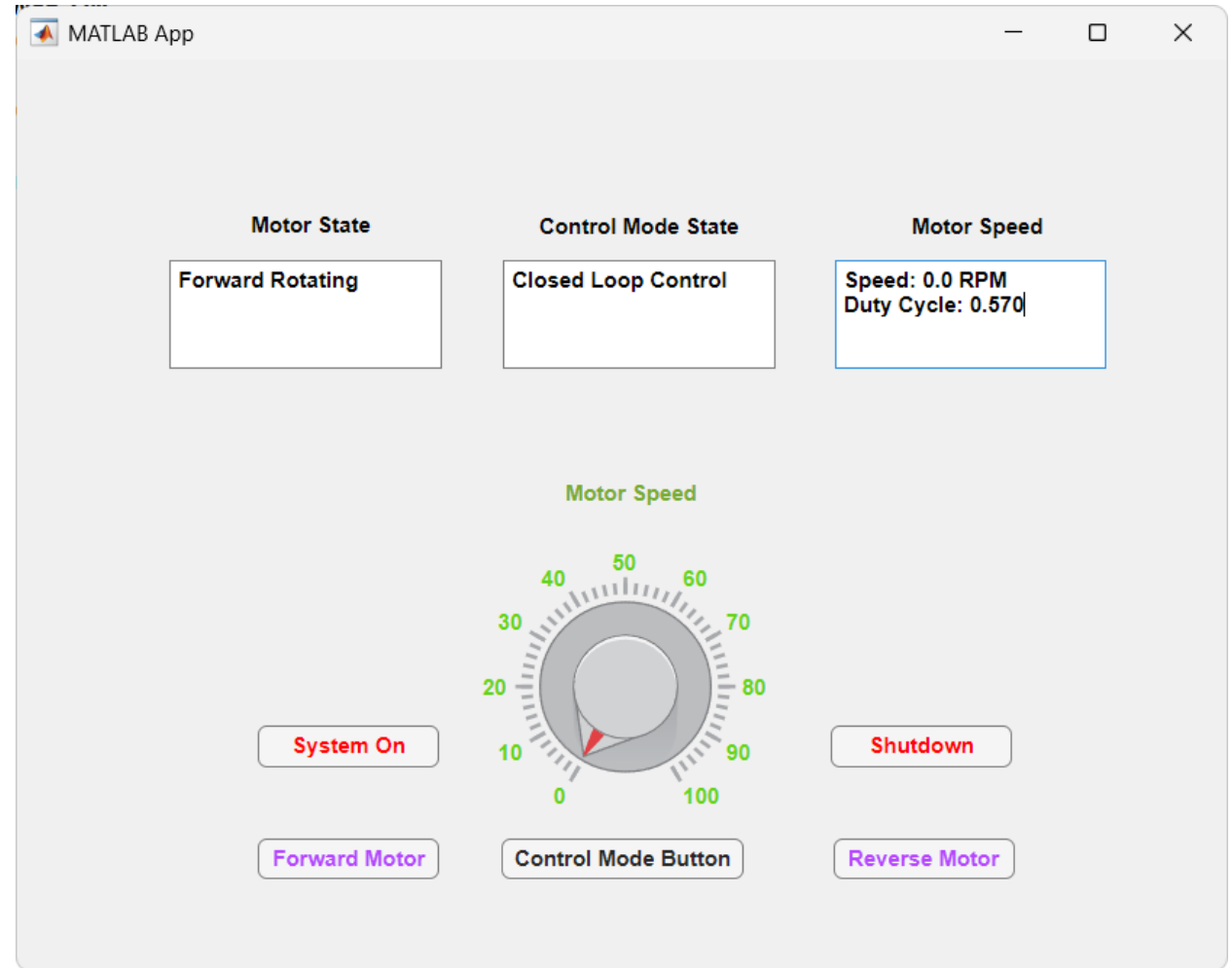


Figure 7: GUI window

Methodology: PWM Generation

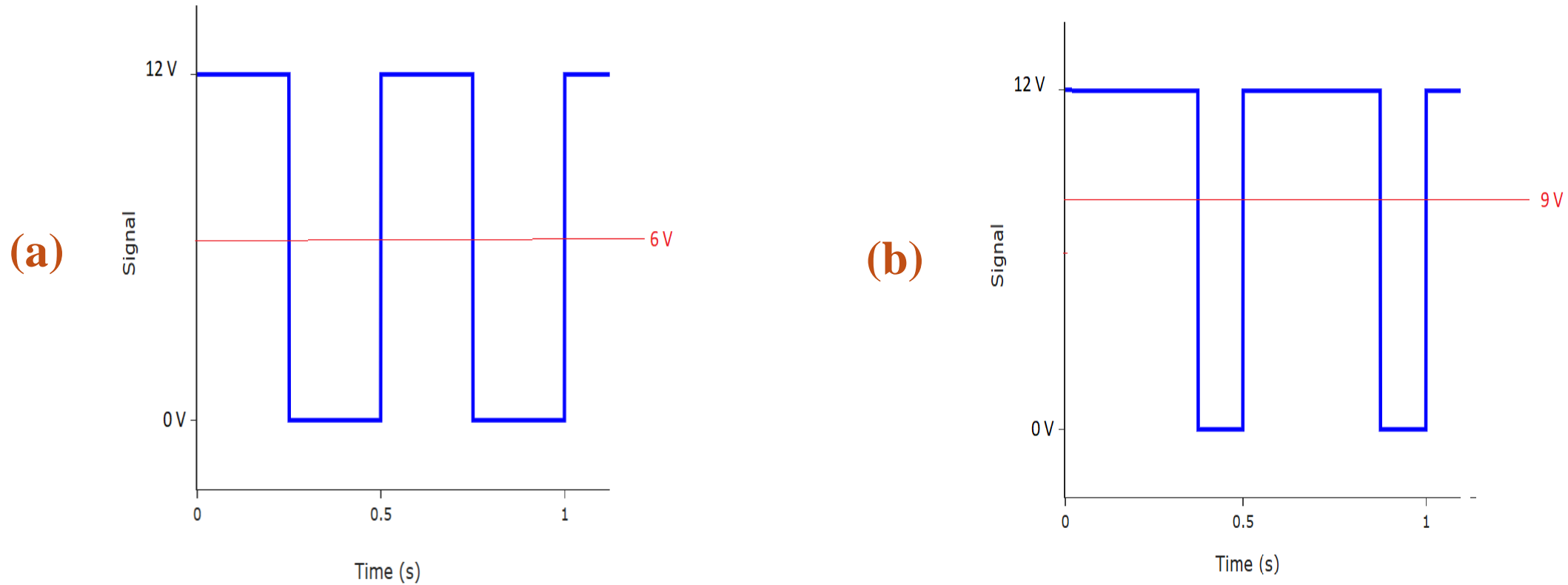


Figure 8: (a) 50% duty cycle that can produce an average voltage of 6V across motor terminals. (b) 75% duty cycle that can produce an average of 9V across motor terminals.

Methodology: PWM Generation

- Arduino **pins 2 and 3** generated **PWM signals** for motor control.
- A **potentiometer** adjusted the **PWM duty cycle**.
- **Pin 3** controlled **forward** and **pin 2** controlled **reverse** rotation.
- **MOSFET driver** translated logic signals to **12 V or 0 V** at motor terminals.
- **Figure 8** shows **50% (≈ 6 V)** and **75% (≈ 9 V)** duty cycles controlling **motor speed**.

Methodology: PID Parameter Tuning

- **PID controller parameters: $K_p = 0.1$, $K_i = 0.4$ and $K_d = 0.01$**
- **Tuned for fast response and minimal speed oscillation.**
- **Ensures motor speed quickly settles to the user-set reference.**

List of Apparatus

Table 1: List of apparatus used in project

S.L No.	Name of Apparatus	Ratings / Specification	Quantity
1	DC power supply	11.5 V, 2 A	1
2	LM2596 DC-DC buck converter	$V_{in} = 11.5 \text{ V}$, $V_{out} = 10.4 \text{ V}$	1
3	Arduino UNO	-	1
4	PC817 optocoupler	$I_F = 50 \text{ mA}$, $I_C = 50 \text{ mA}$, $V_{CEO} = 35 \text{ V}$	2
5	IRFZ44N MOSFET	-	4
6	1N4007 diode	$V_{PIV} = 1000 \text{ V}$, $V_F = 0.7 \text{ V}$	1
7	DC motor (dynamo)	4–12 V, 4500 rpm	1
8	DC generator (dynamo)	4–12 V, 4500 rpm	1

List of Apparatus

S.L No.	Name of Apparatus	Ratings / Specification	Quantity
9	Resistor	220 Ω , 2.2 k Ω , 10 k Ω , 100 k Ω (0.25 W) – 5 each ; 15 Ω , 18 Ω (10 W) – 1 each	-
10	Potentiometer	1 k Ω , 100 k Ω , 1 W	1 each
11	Relay switch	Vtrigg = 5 V	3
12	Rocker switch	3 A	1
13	Push buttons	0.5 mA	3
14	Fuse	10 A	1
15	Multimeter	0–50 V DC	1
16	Breadboard	-	3
17	Jumper wires and probes	-	As needed

Model Description: Proteus Blueprint

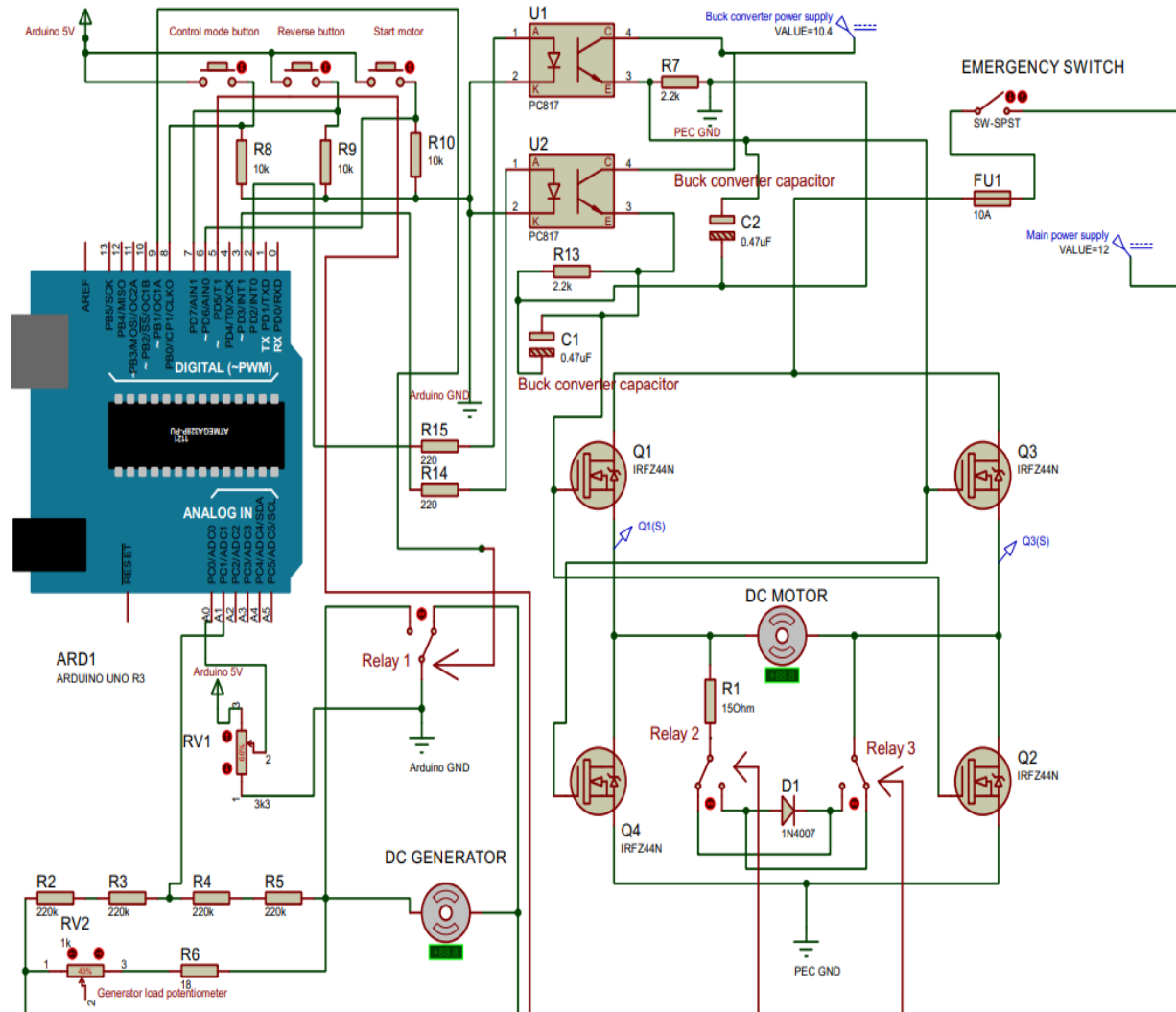


Figure 9: Circuit diagram of the whole prototype

Model Operation: Motor Rotation

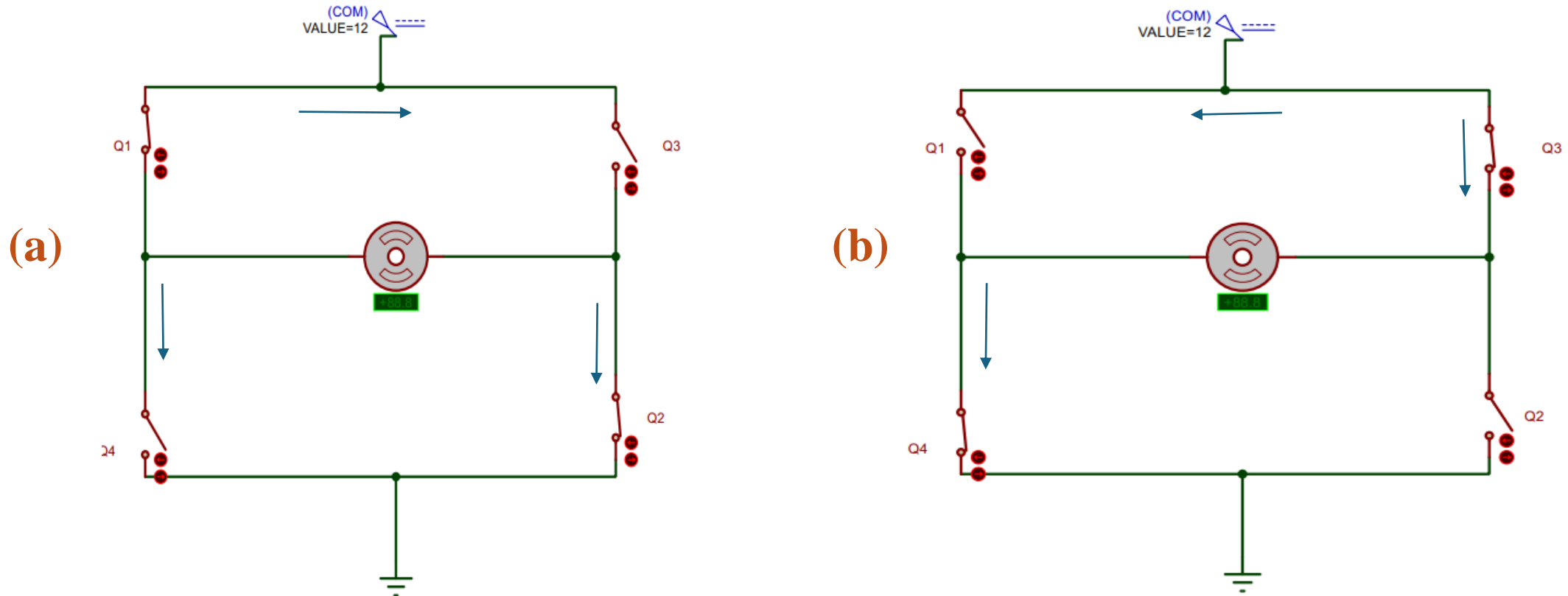


Figure 10: Equivalent single pole single throw (SPDT) switch circuit of H-bridge converter motor drive for the case of (a) Forward motoring and (b) reverse motoring. Blue arrows show current flow.

Model Operation: Monitoring

- **Potentiometer** on analog **pin A0** acts as both **accelerator and brake**
- Motor speed increases or decreases based on potentiometer rotation direction
- **50% duty cycle** (minimum) ensures smooth running and **prevents shutdown below 4 V**
- 100% duty cycle gives maximum motor speed
- **Reverse motion** is controlled via a dedicated **reverse gear button in the GUI.**

Model Operation: Control Modes

- Motor control mode can be toggled **between open and closed loop** via a **control mode button**
- In open loop mode, **speed varies with load changes** since **no feedback** is used
- **Increased load slows the motor** and **reduced load speeds it up** even at **fixed input**
- This behavior **mirrors real EV acceleration on uneven terrain**; hence, **feedback control** is essential for stable motor speed **under varying load**.

Model Operation: Open Loop Action

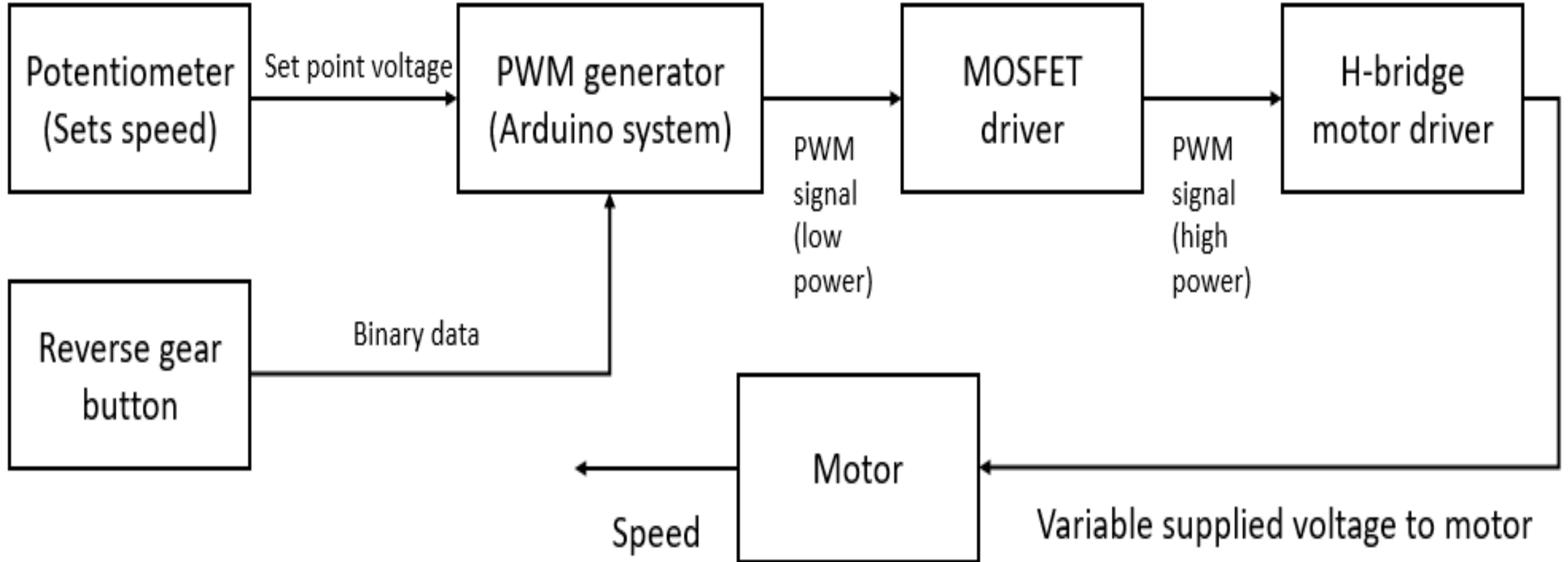


Figure 11: Open loop control of motor speed.

Model Operation: Closed Loop Action

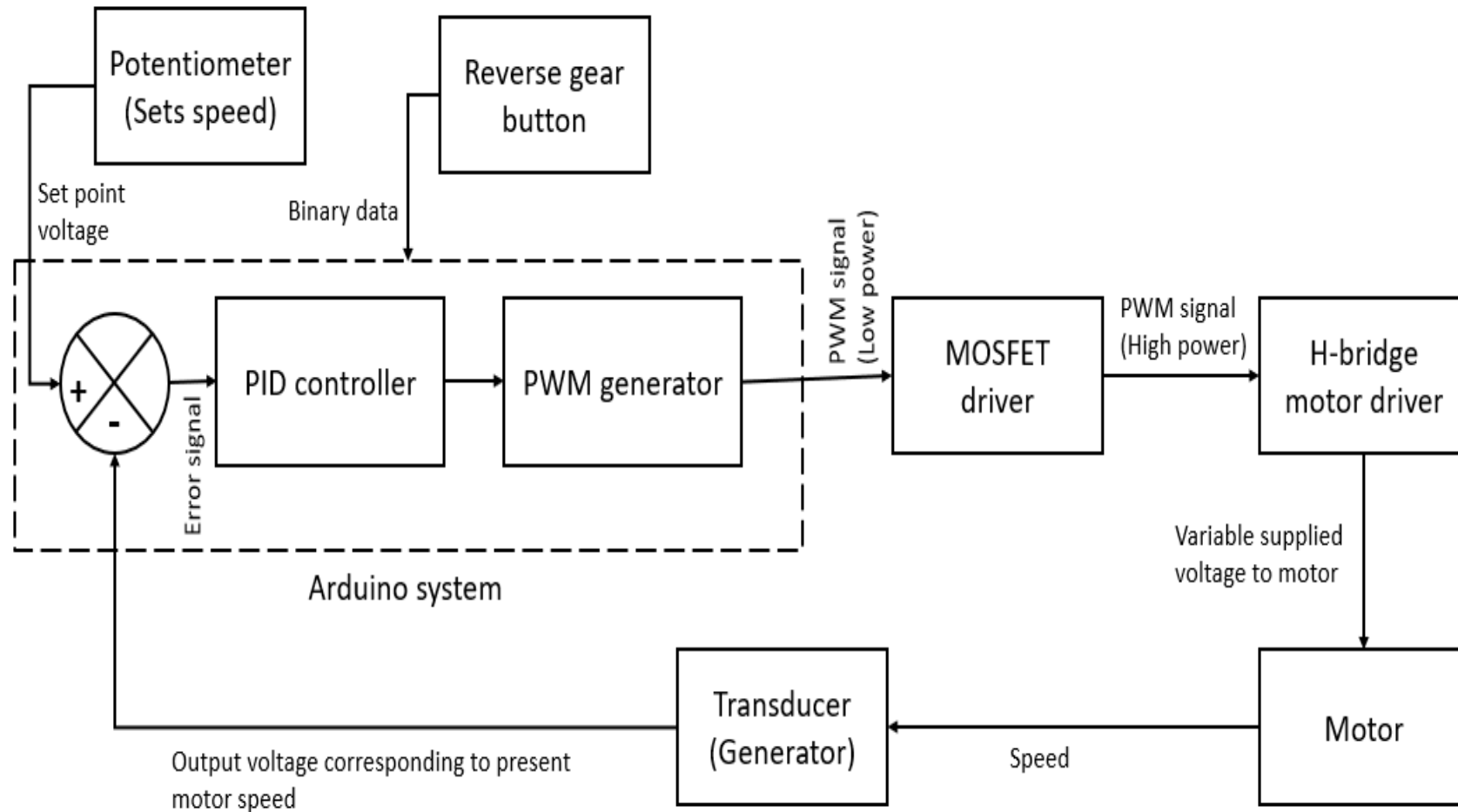


Figure 12: Closed loop control of motor speed

Results: Overview

Table 2: Overview of prefixed data

S.L. no.	Name of data	Value
1	Time period of PWM signal	30ms
2	Frequency of PWM signal	33.33 Hz
3	Buck converter output	10.4 (approx.)
4	Duty cycle of PWM for lowest motor speed	50 % (regular operation), 0% (open loop test), 50% (closed loop test)
5	Duty cycle of PWM for highest motor speed	100 %

Results: Open Loop Test

Table 3: Summary of open loop test

S.L no.	Parameter name	Value
1	Maximum motor terminal voltage	7.35V (approx.)
2	Minimum motor terminal voltage just before motor stops (for 40% duty cycle)	4V (approx.)
3	Maximum voltage across generator terminal (this corresponds to maximum motor speed)	5.5 V (approx.)
4	Minimum voltage across generator terminal just before motor stops (this corresponds to minimum motor speed at 40% duty cycle)	2.06 V (approx.)

Results: Motor-Generator Terminal Voltage Comparison

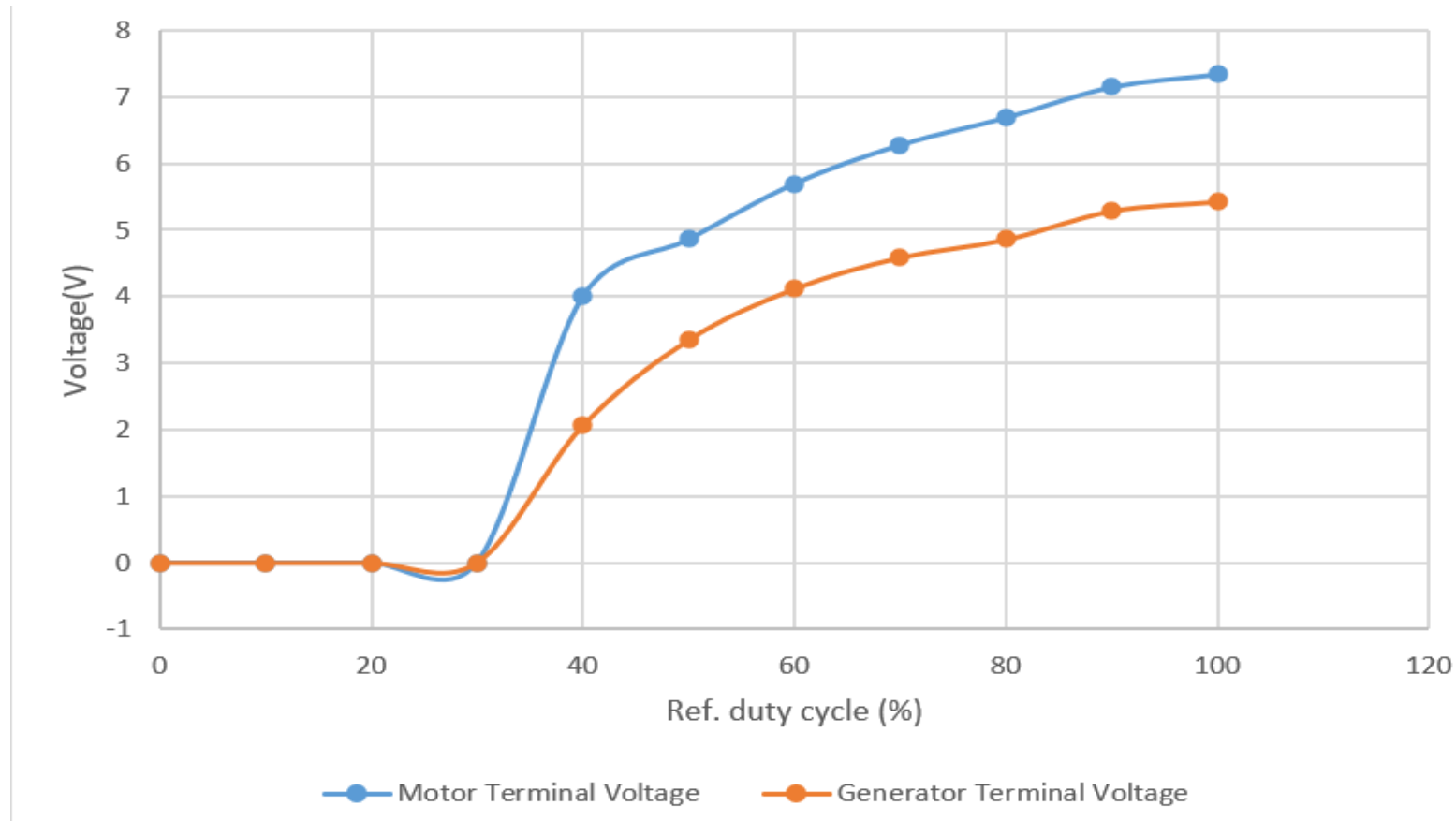


Figure 13: Motor–generator voltage comparison showing lower generator voltage, indicating frictional losses from coupling faults.

Results: Motor-Generator Terminal Voltage Comparison

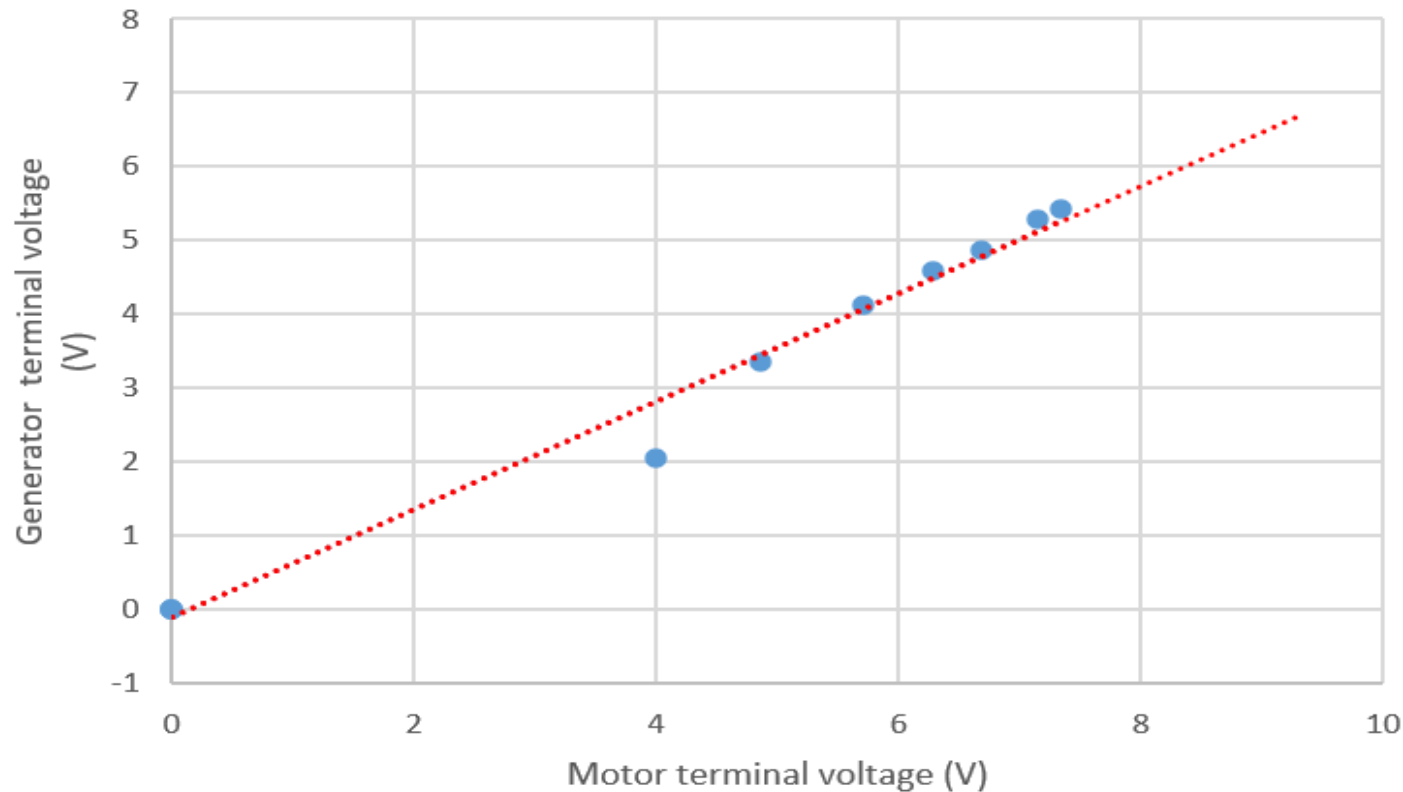


Figure 14: Linear trend relation between motor and generator terminal voltage. To measure motor speed correctly, the generator voltage should have a linear link with motor speed which in turns is expressed by motor terminal voltage.

Results: Closed Loop Test

Table 4: Summary of closed loop test

S.L no.	Parameter name	Value
1	Maximum voltage across generator terminal (this corresponds to maximum motor speed)	4.8 V (approx.)
2	Minimum voltage across generator terminal (this corresponds to minimum motor speed at 50 % duty cycle)	3.3 V (approx.)

Results: Variations of Duty Cycle

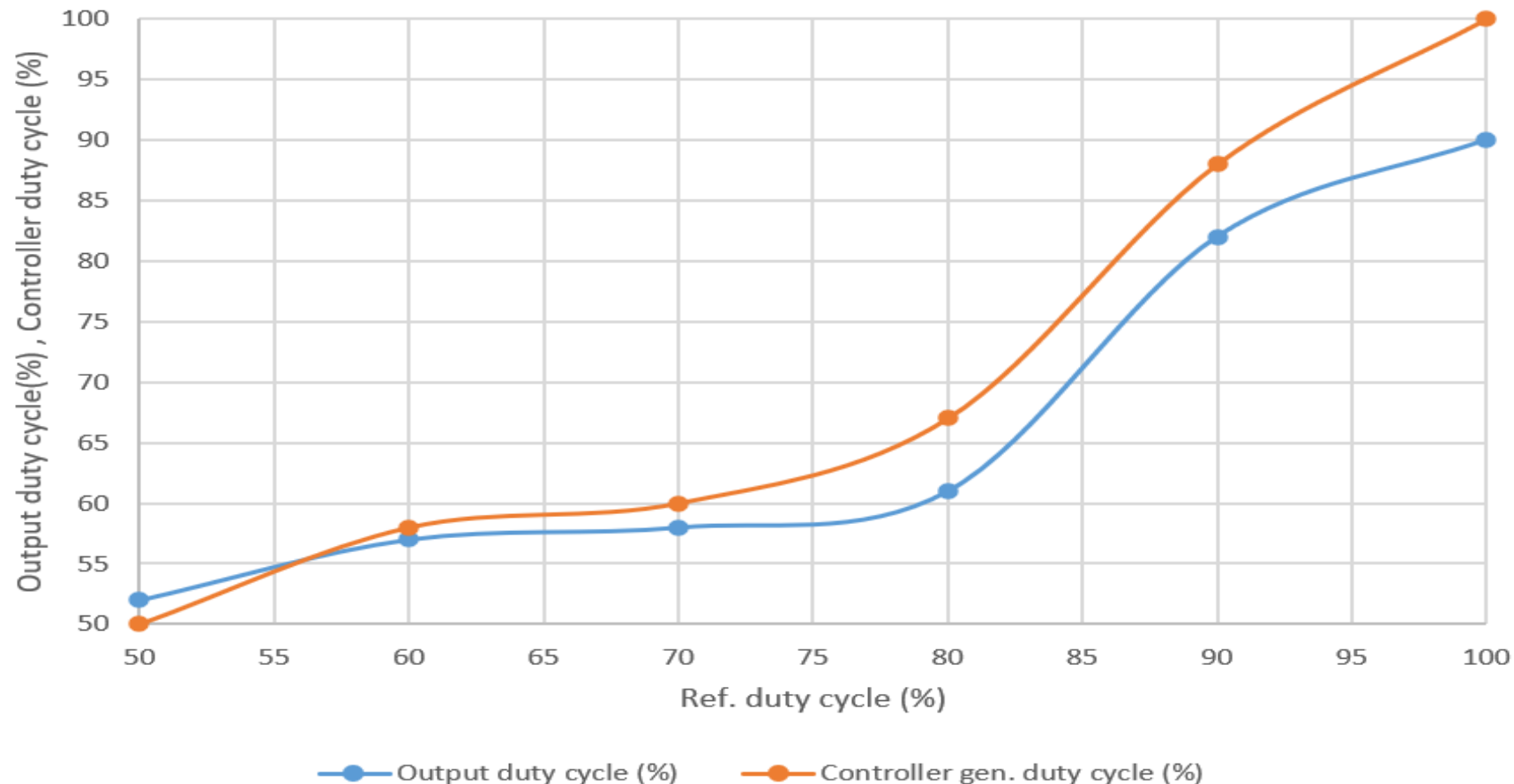


Figure 15: Variation of output and controller gen. duty cycle with ref. duty cycle

Results: PID Response Characteristics

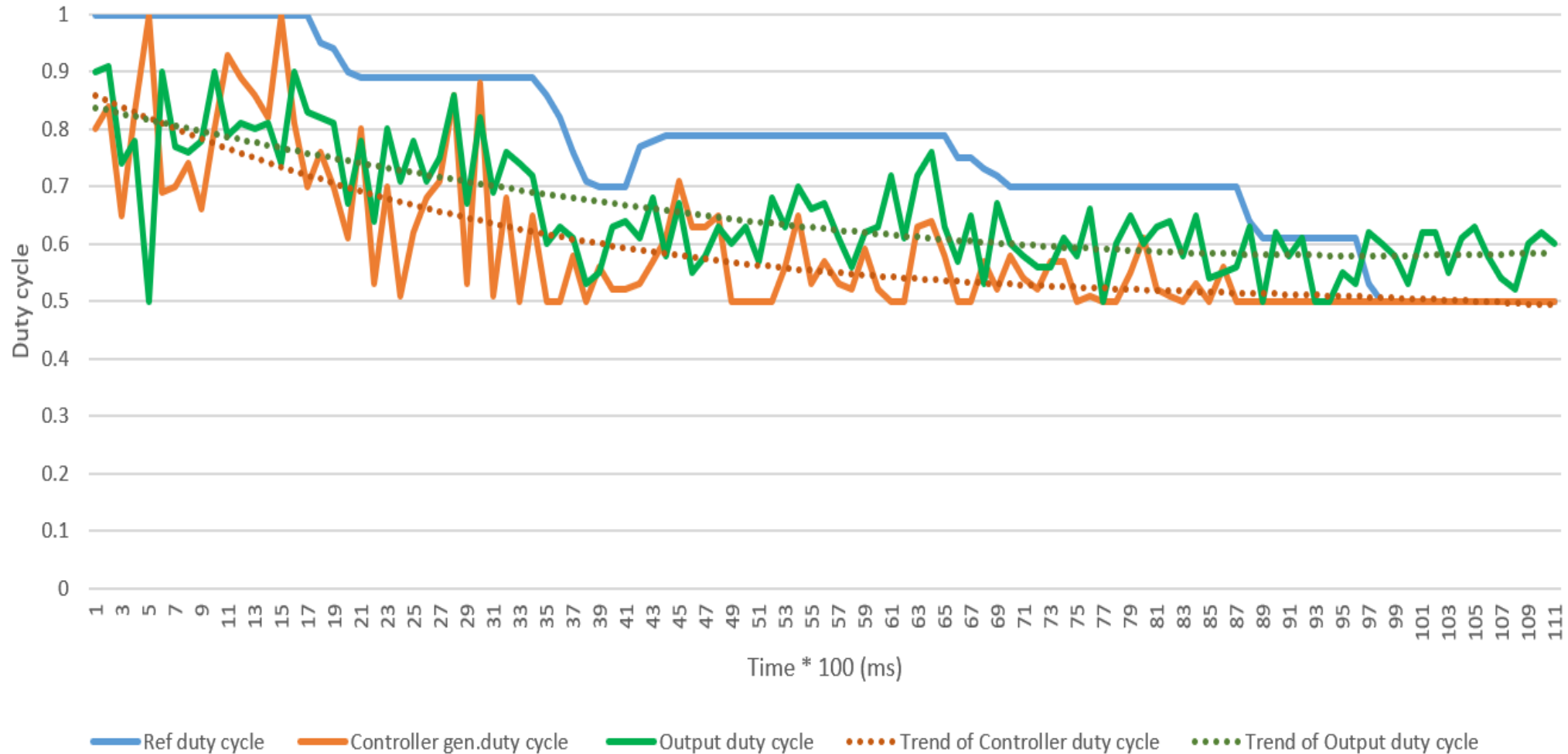


Figure 16: Real time data of PID response

Results: Calibration of Parameters

Table 5: List of calibrated Data

S.L no.	Name of Data	Calibrated value
1	Microcontroller ADC output for maximum generator output voltage	640
2	Proportional gain of PID controller, K_p	0.1
3	Integral gain of PID controller, K_i	0.4
4	Derivative gain of PID controller, K_d	0.01

Conclusion

- **H-bridge** driver prototype successfully drives **DC motors for Evs**
- It can operate in **both open and closed** loop control modes
- The design allows **excess inductive power to be transferred to an auxiliary low power source**
- Performance is **satisfactory** but design **improvements are possible**
- Using a **non-invasive speed sensor** instead of a generator **could reduce energy loss** from coupling faults.

Thank You

Any Questions?

